
Lab 3: Push-Pull Power Amplifier

Student Names: Deniz Uzun, Callum Mckelvie, Kimberley Orna

Student Number: 1006035005, 1006401314, 1006002709

Preparation

1. Determine the value of C_s for the cut-off frequency of 50 Hz or less ($f_{3dB} = 1/2\pi R_L C_s$). The power stage can be assumed as a dependent voltage source with zero output impedance. Show your hand calculation. Show your hand calculation.

$$1) f_{3dB} = 50 \text{ Hz}$$

$$f_{3dB} = \frac{1}{2\pi R_L C_s}$$


$$C_s = \frac{1}{2\pi R_L f_{3dB}}$$

$$= \frac{1}{2\pi (8)(50)}$$

$$= \frac{1}{800\pi}$$

$$= 0.398 \text{ mF}$$

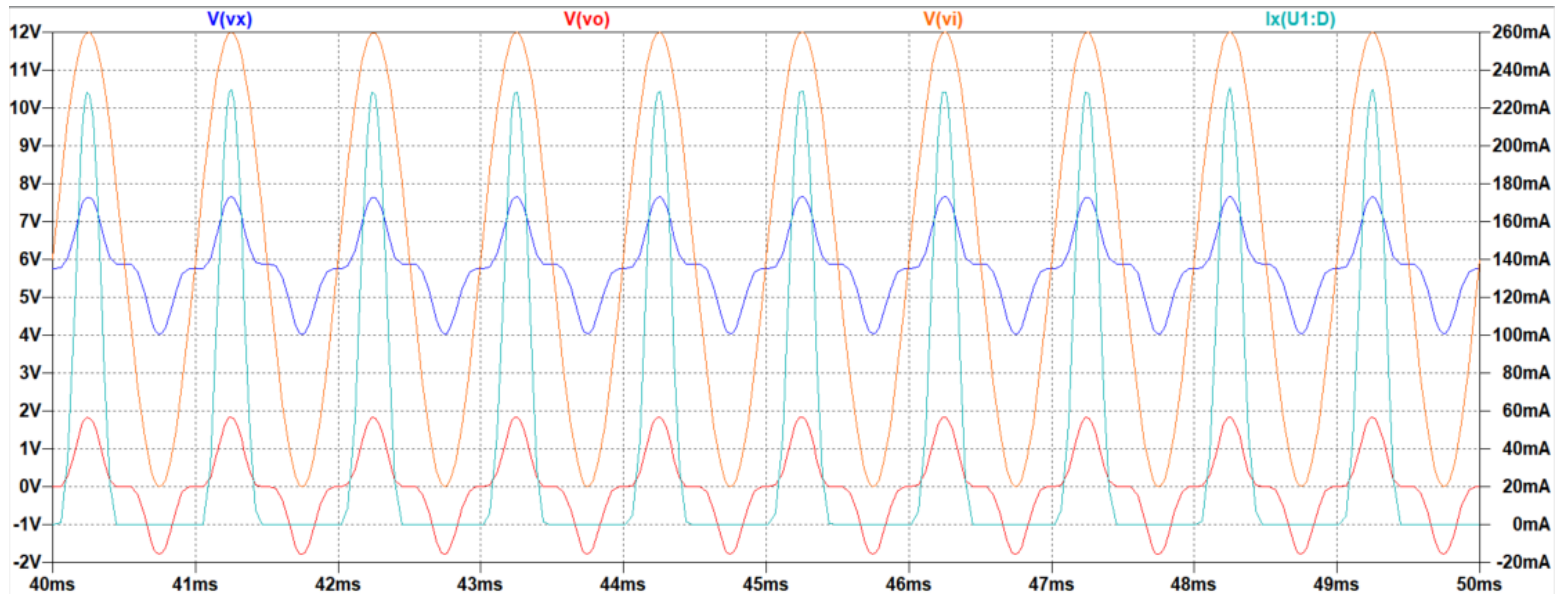2. Simulate the class-B push-pull power amplifier in Figure 1(a) with a 1-kHz 12-V_{pp} sinusoid input biased at 6 V and plot V_i , V_x , V_o , and I_{D1} . Simulate the circuit long enough (about 50 ms) to let C_s settle and zoom in to the portion close to the end of the simulation to show a few cycles of the sinusoid.



3. Determine the value of V_{OS} and R_1 in Figure 1(c) required to cancel the dead zone using the plot in the previous step.

$$|V_{tp}| = |7.637 - 11.977| = 4.34 \text{ V}$$



$$V_{tn} = 4.038 - 4.067 \times 10^{-3} = 4.034 \text{ V}$$

$$V_{os} = V_{tn} + |V_{tp}| = 8.374 \text{ V}$$

$$R_1 = V_{os} / I_{d4} = 8.314 / 1 \times 10^{-3} = 8.314 \text{ k}\Omega$$

***CORRECT VALUE IS 7.2 k Ω ***

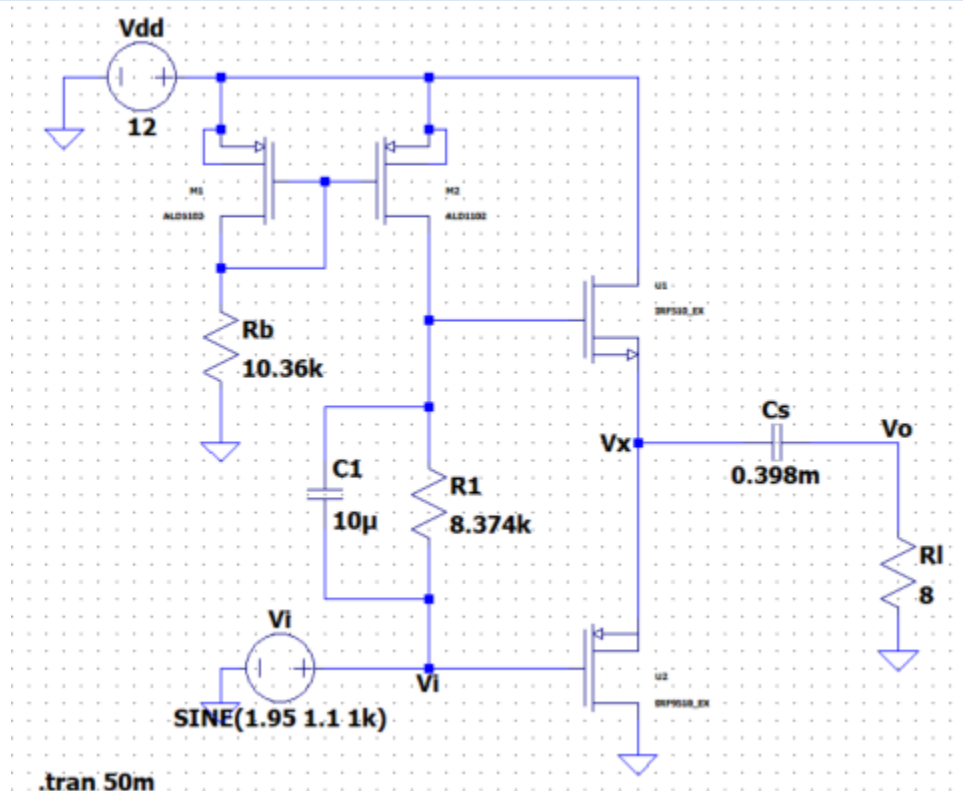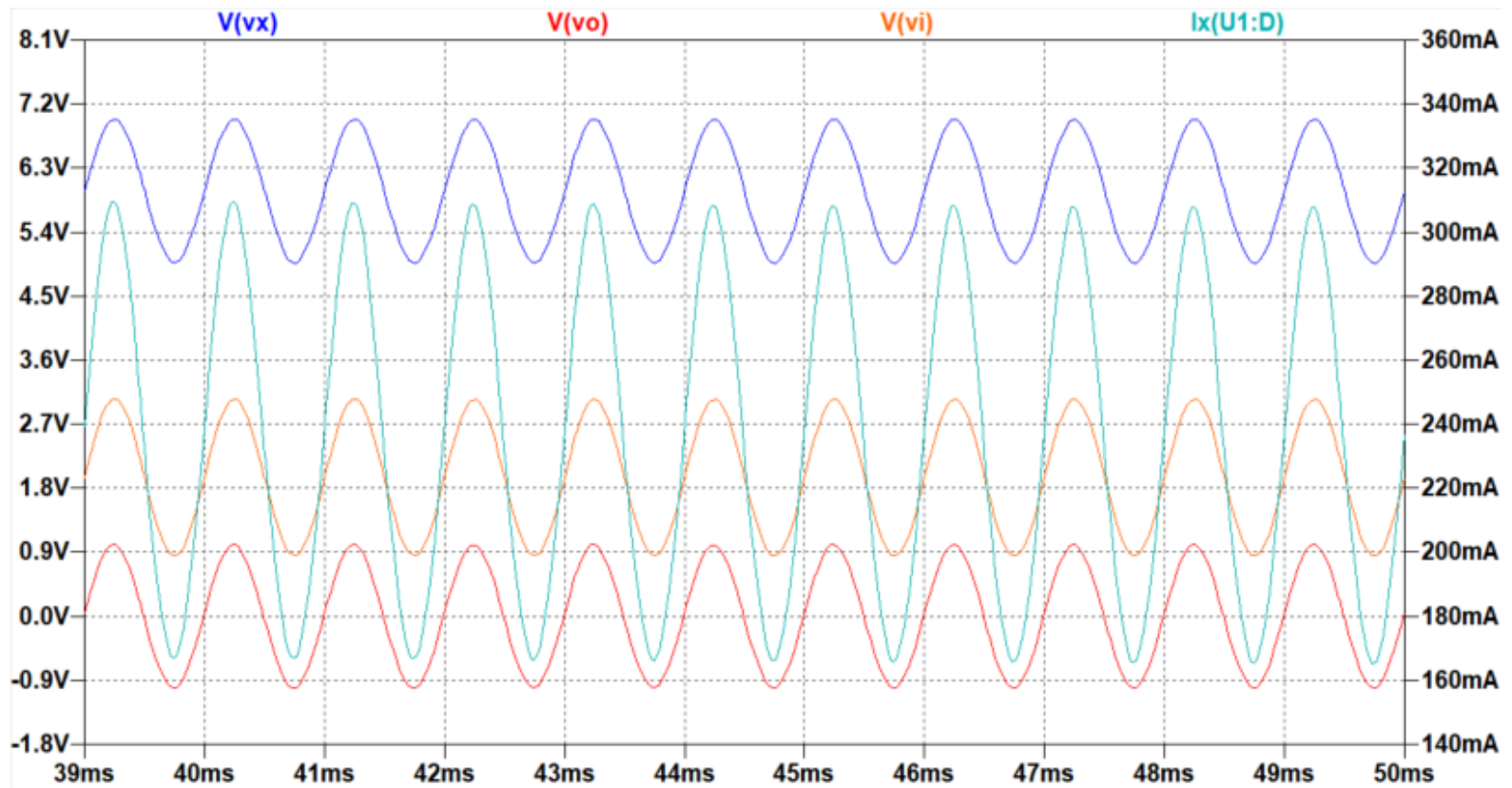4. Simulate the class-AB push-pull amplifier in Figure 1(c) using the value of R_1 found in the previous step. Adjust the input signal source such that the output node, V_x is biased at 6 V with a 2-V_{pp} swing. Plot V_i , V_x , V_o , and I_{D1} . Simulate the circuit long enough (about 50 ms) to let C_s settle, and zoom in to the portion close to the end of the simulation to show a few cycles of the sinusoid. Make sure that the power transistors are biased just in class-AB region so the power consumption is kept minimum while the dead zone is cancelled. This step requires fine tuning of R_1 as well as the input signal source.



5. Determine the voltage gain of the power amplifier


$$A_v = V_{out_{pp}} / V_{in_{pp}} = -2.016 / 2.2 = -0.916 \text{ V/V}$$

Lab - Part II: Class AB Power Amplifier Implementation

3. Adjust R_1 to put the amplifier just in the class-AB mode. This can be done by increasing R_1 and thus V_{OS} from its minimum while applying an input signal and monitoring the output on the oscilloscope until the dead zone disappears.

$$V_{OS} = 6.92 \text{ V}$$

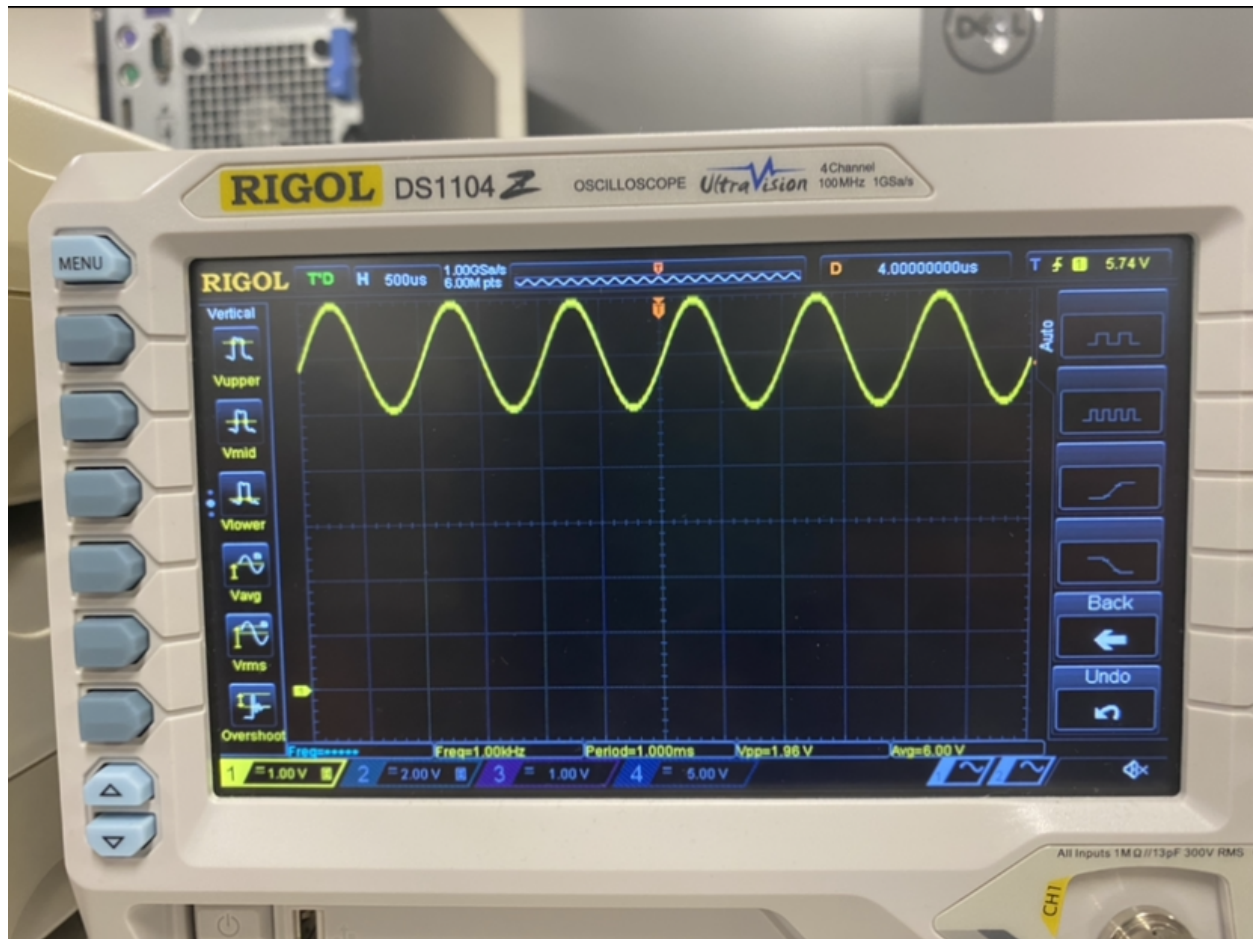4. Adjust the signal generator for a 1-kHz 2-V_{pp} sinusoid biased at 6 V at the output. Show the waveforms.



5. Determine the voltage gain of the power amplifier

$$V_{opp} = 1.96 \text{ V}$$

$$V_{ipp} = 2.6 \text{ V}$$

$$A_v = V_{opp} / V_{ipp} = 1.96 / 2.6 = 0.754 \text{ V/V}$$