
Lab 4: Operational Amplifier

Student Name: Deniz Uzun

Student Number: 1006035005

Preparation

2) Find the numerical values for A_d , A_c , CMRR, and f_{3dB} for $I_B=1mA$ and $C_L=1nF$. Show hand calculations.



$$A_d = -65.1 \text{ V/V} = 36.3 \text{ dB}$$

$$A_c = 4.31 \text{ mV/V} = -47.3 \text{ dB}$$

$$\text{CMRR} = A_d/A_c = 15103 \text{ V/V} = 83.6 \text{ dB}$$

$$f_{3dB} = 5.183 \text{ kHz}$$

(See the hand calculations below.)

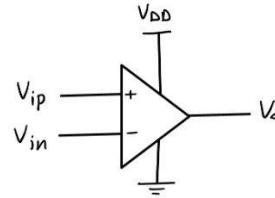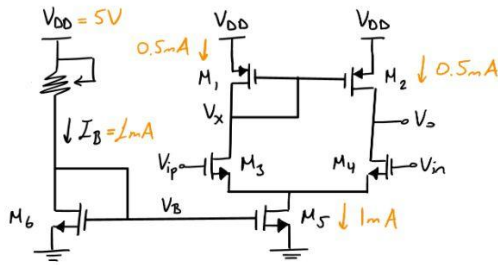

$$g_m = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right) I_{DS}}$$

$$\text{NMOS } \mu_n C_{ox} \left(\frac{W}{L}\right) = 4.49 \text{ mA/V}^2$$

$$g_{m4} = \sqrt{2 \cdot (4.49 \cdot 10^{-3}) \cdot 0.5 \cdot 10^{-3}} \\ = 0.00212 = 2.12 \text{ mA/V}$$

$$\text{PMOS } \mu_p C_{ox} \frac{W}{L} = -2.10 \text{ mA/V}^2$$

$$g_{m2} = \sqrt{2 \cdot (-2.10 \cdot 10^{-3}) \cdot (-0.5) \cdot 10^{-3}} \\ = 0.00145 = 1.45 \text{ mA/V}$$

$$r_o = \frac{|V_A|}{I_{DS}}$$

$$|V_A|_{\text{NMOS}} = 80 \text{ V}$$

$$|V_A|_{\text{PMOS}} = 19 \text{ V}$$

$$r_{o2} = \frac{19 \text{ V}}{0.5 \text{ mA}} = 38 \text{ k}\Omega$$

$$r_{o4} = \frac{80 \text{ V}}{0.5 \text{ mA}} = 160 \text{ k}\Omega$$

$$r_{o5} = \frac{80 \text{ V}}{1 \text{ mA}} = 80 \text{ k}\Omega$$

$$A_d = -g_{m4} (r_{o4} \parallel r_{o2}) = -2.12 \cdot 10^{-3} (160 \cdot 10^3 \parallel 38 \cdot 10^3) \\ = -65.1 \text{ V/V} = \boxed{36.3 \text{ dB}}$$

$$A_c = -g_{m4} r_{o4} \frac{\frac{1}{g_{m2}}}{2g_{m4} r_{o4} r_{o5} + \frac{1}{g_{m2}}} \approx -\frac{1}{2g_{m2} r_{o5}}$$


$$\approx -\frac{1}{2 \cdot (1.45 \text{ mA}) \cdot 80 \text{ k}\Omega} = 4.31 \cdot 10^{-3} \text{ V/V} = \boxed{-47.3 \text{ dB}}$$

$$\frac{A_d}{A_c} = 2g_{m2} g_{m4} r_{o5} (r_{o4} \parallel r_{o2}) = 2 (1.45 \text{ mA}) (2.12 \text{ mA}) \cdot 80 \text{ k}\Omega \cdot (160 \text{ k}\Omega \parallel 38 \text{ k}\Omega) \\ = 15103 \text{ V/V} = \boxed{83.6 \text{ dB}}$$

$$f_{3dB} = \frac{1}{2\pi (r_{o4} \parallel r_{o2}) C_L} = \frac{1}{2\pi (160 \text{ k}\Omega \parallel 38 \text{ k}\Omega) 1 \text{ nF}} = 5183 \text{ Hz} = \boxed{5.18 \text{ kHz}}$$

3) Find the input common-mode voltage that maximizes the output swing. Show hand calculations.

$$V_{CM} = 1.85 \text{ V}$$

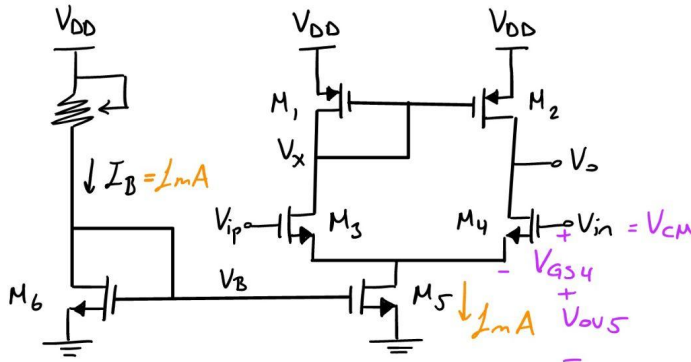

$$V_{CM} = V_{OV5} + V_{GS4}$$

$$V_{OV5} = \sqrt{\frac{2I_{D5}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} = \sqrt{\frac{2 \cdot 1 \text{ mA}}{4.49 \text{ mA/V}^2}} = 0.667 \text{ V} = 667 \text{ mV}$$


$$V_{GS4} = V_{OV4} + V_{TNMOS}$$

$$V_{OV4} = \sqrt{\frac{2 \cdot 0.5 \text{ mA}}{4.49 \text{ mA/V}^2}} = 0.472 \text{ V} = 472 \text{ mV} \quad V_{TNMOS} = 0.71 \text{ V}$$


$$V_{GS4} = 0.472 \text{ V} + 0.71 \text{ V} = 1.182 \text{ V}$$

$$V_{CM} = 667 \text{ mV} + 1.182 \text{ V} = 1.849 \text{ V} \approx 1.85 \text{ V}$$

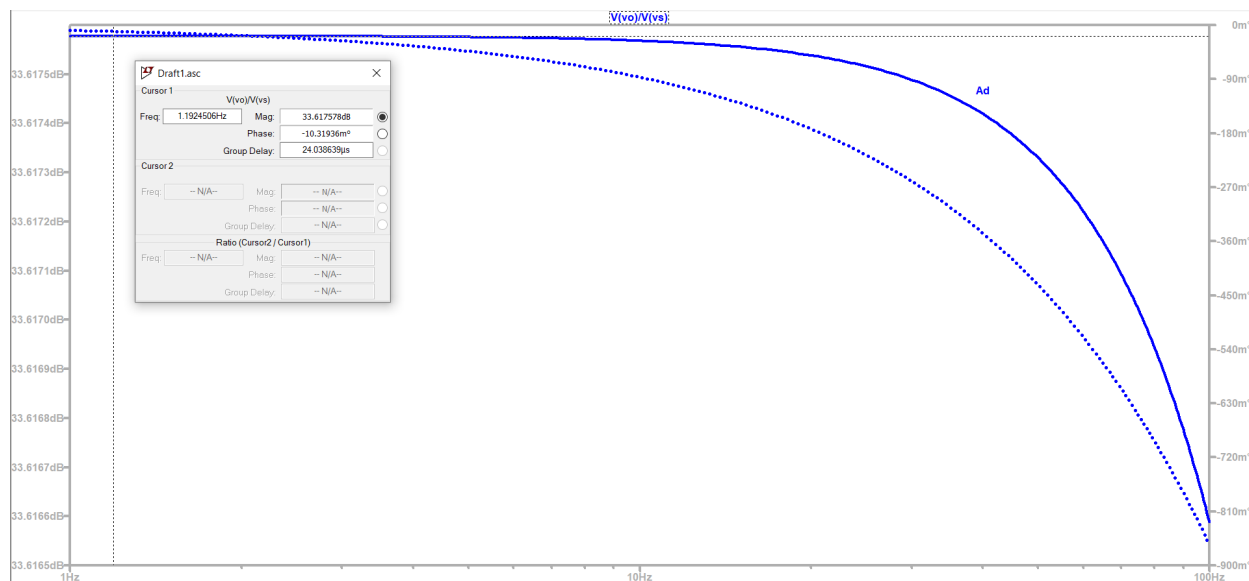
5) Run AC simulations to show A_d , A_c and CMRR at low frequencies. Also run a DC simulation to show the output swing with a differential input with the common-mode voltage found in 3. Label and comment on the plots to clearly show the results.



$A_d = 33.6 \text{ dB}$

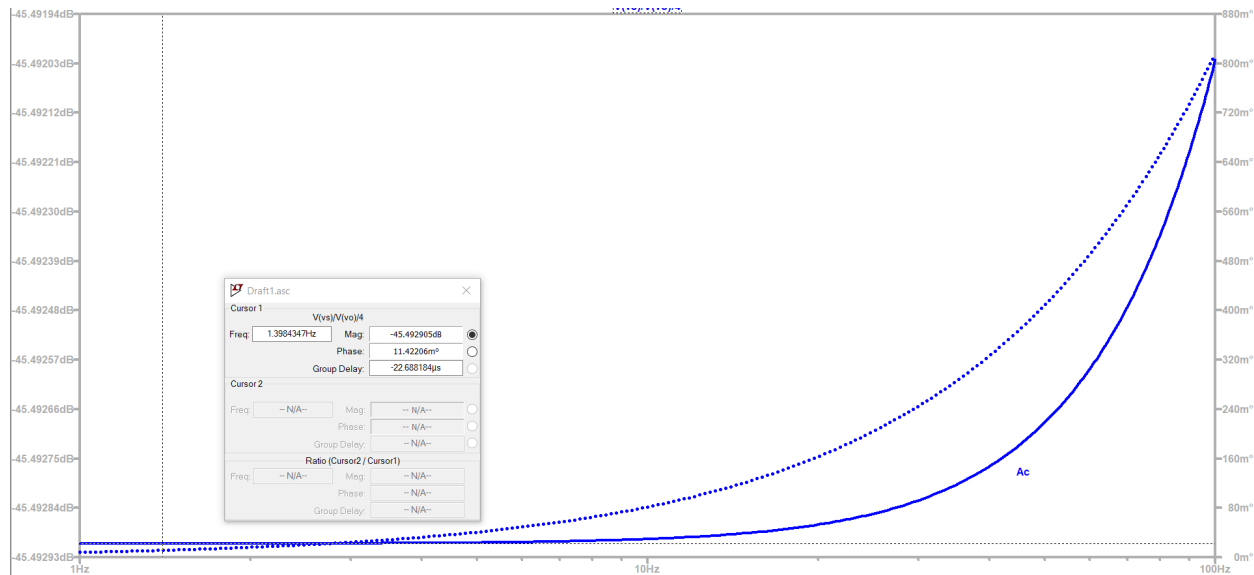


$A_c = -44.5 \text{ dB}$

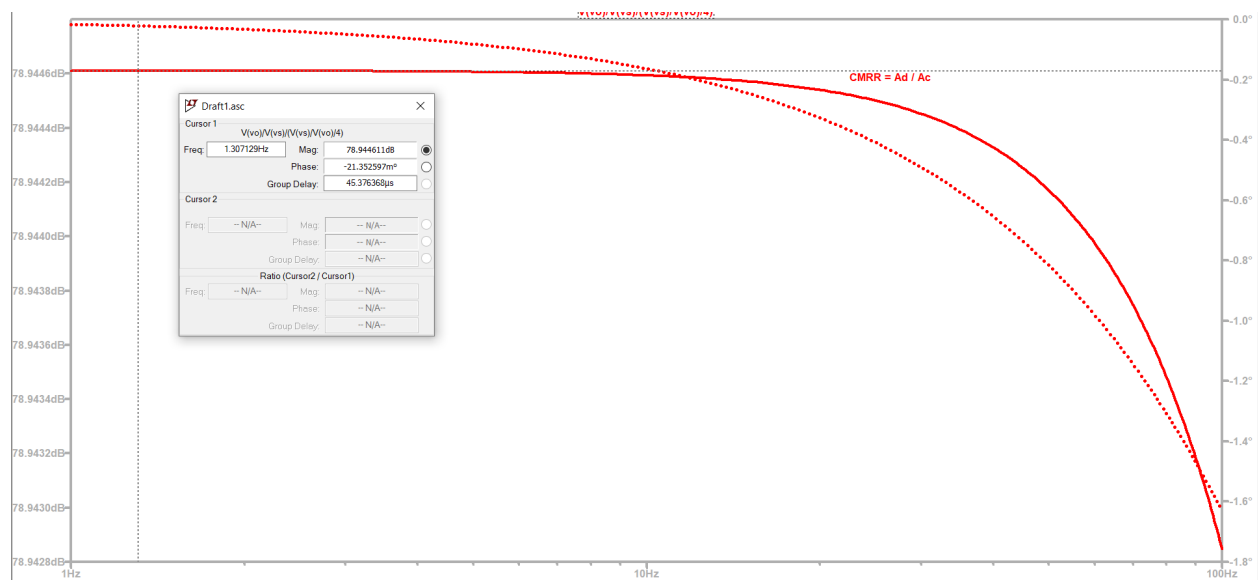

CMRR: 78.9 dB

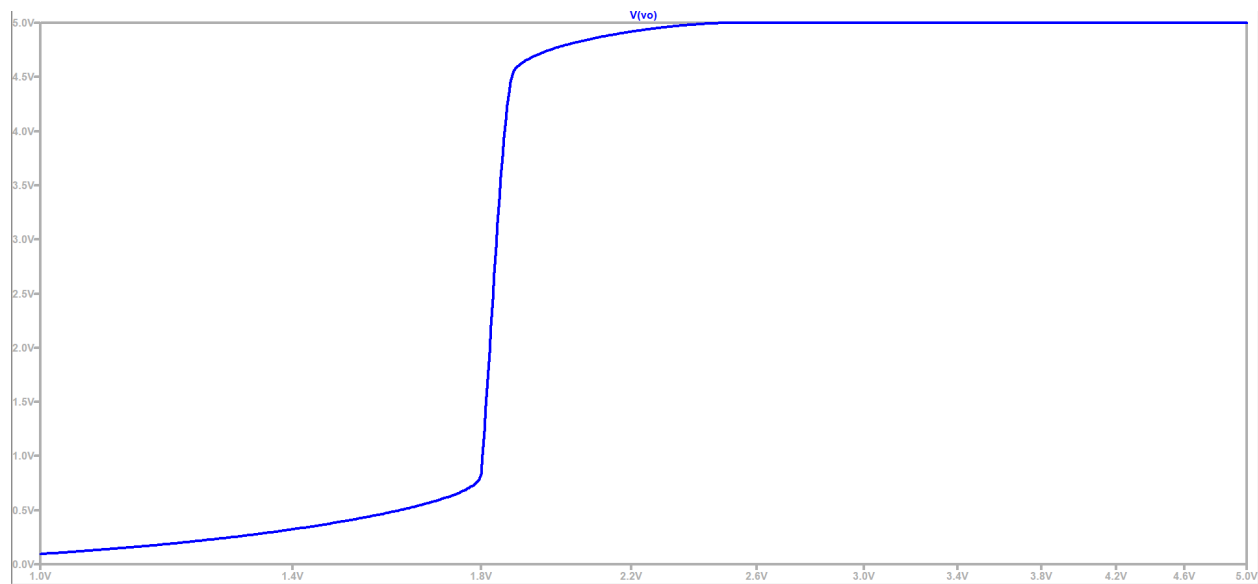
Output swing with a differential input with $A_{cm} = 1.85$ dB



Lab

2. Experiment

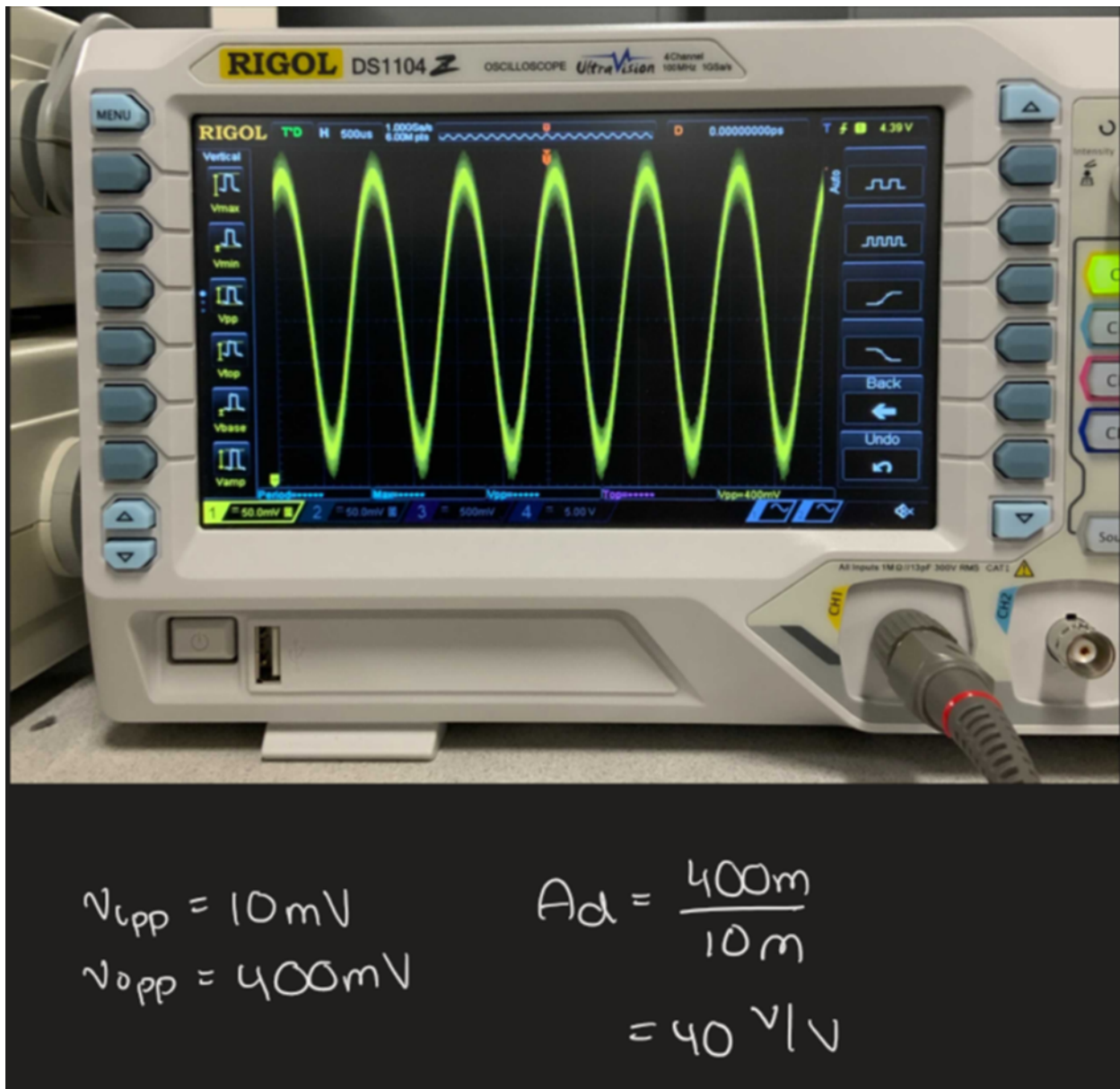- 4) Connect one of the opamp inputs to a signal generator via a large capacitor as shown in Figure 3(b) and find the differential gain (A_d) of the opamp.



Final answer: $40 \text{ V/V} = 32 \text{ dB}$

Final answer: 40 V/V – less than theoretical value due to losses in the cct (wire resistance, potentiometer, leads for the input/output signals)