

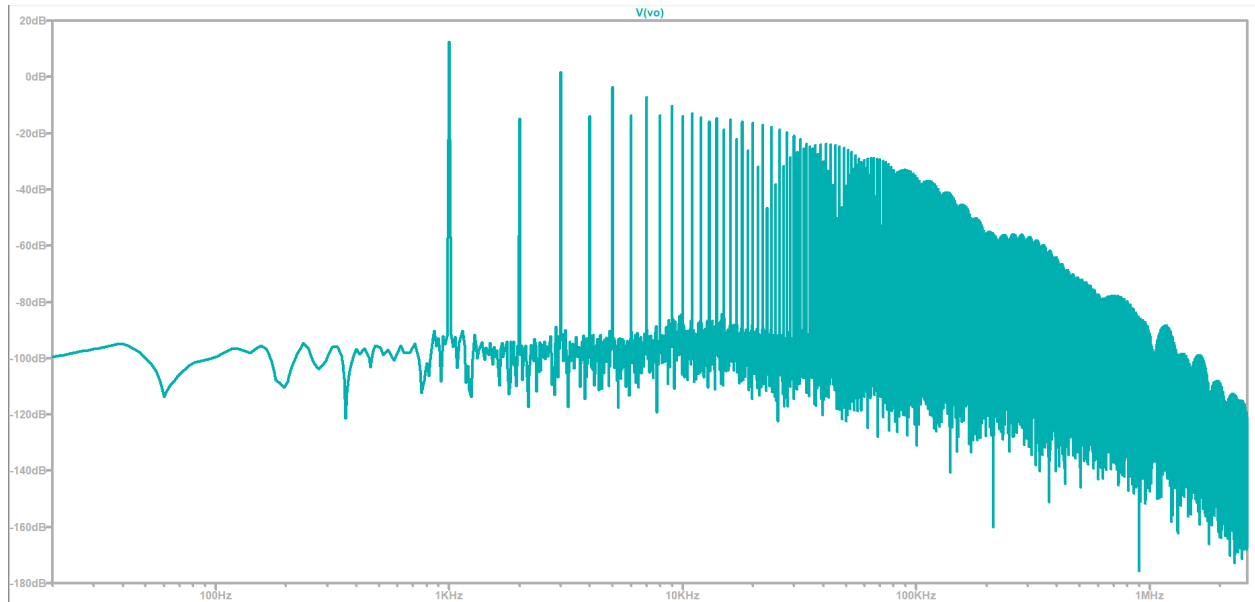


Preparation

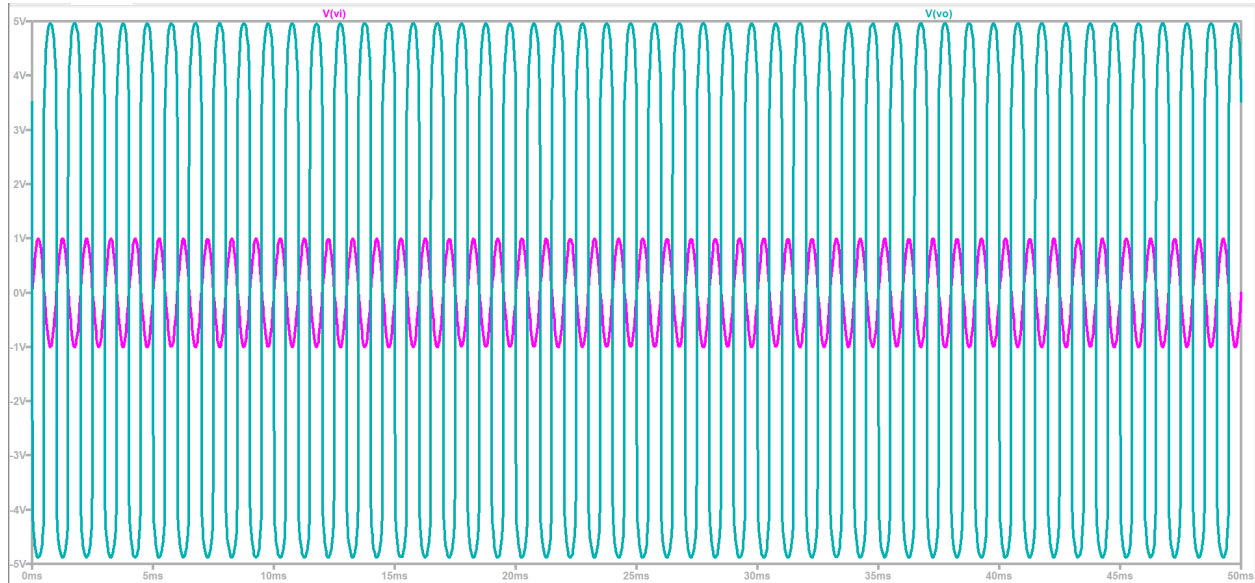
1. Run a 50-ms transient simulation for the Class-A output stage in Figure 2 (a) with 1-kHz 1-V_{pp} input. Show the input voltage and output voltage waveform. Set the maximum time step of the transient simulation to 1 μ s. Plot the output spectrum using the FFT function of the simulator. Find the power consumption of the amplifier when the input signal amplitude is 10 mV_{pp} and when it is 1 V_{pp}.



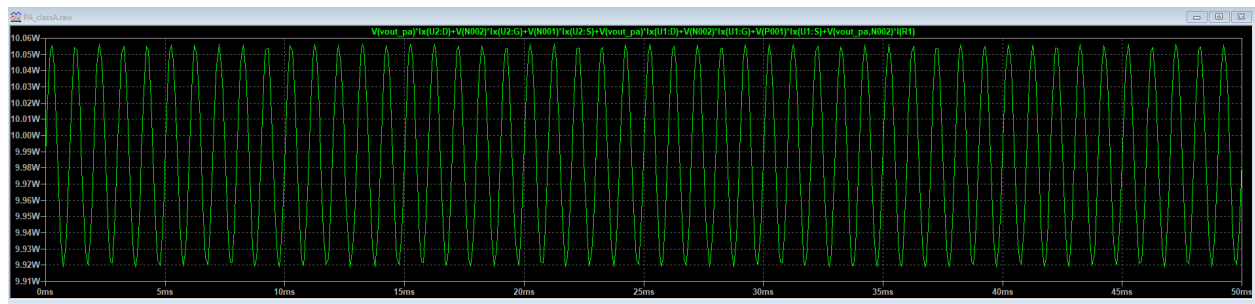
Power consumption when input signal amplitude is 10 mVpp



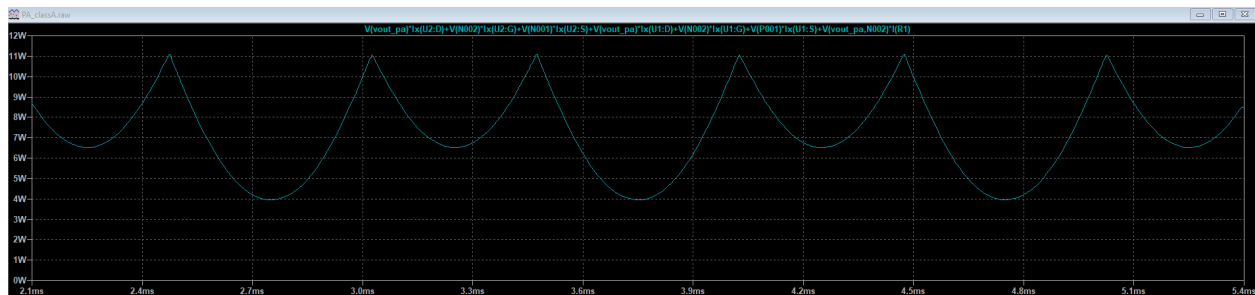Power consumption when input signal amplitude is 1Vpp




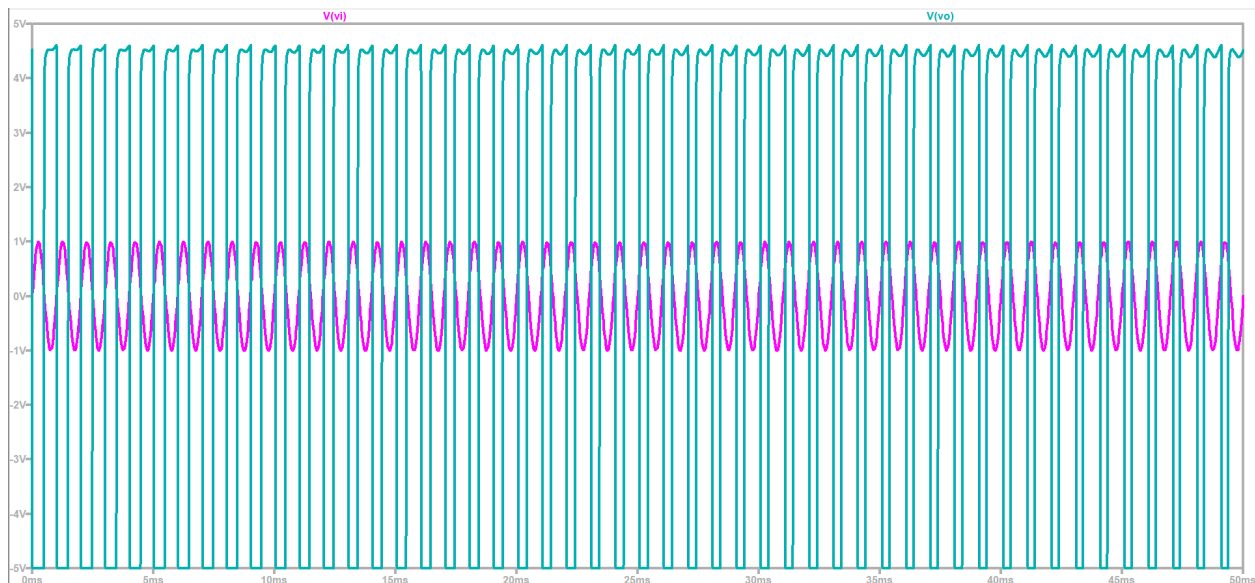2. Repeat step 1 for the Class-B output stage in Figure 2 (b). Use the value for R1, R2, R3, and R4 determined in lab 3 such that both the p-MOSFET and the n-MOSFET are biased at threshold (little or no current flowing through them).




Input between -0.5V and 0.5V


Output saturates at -5V and 5V

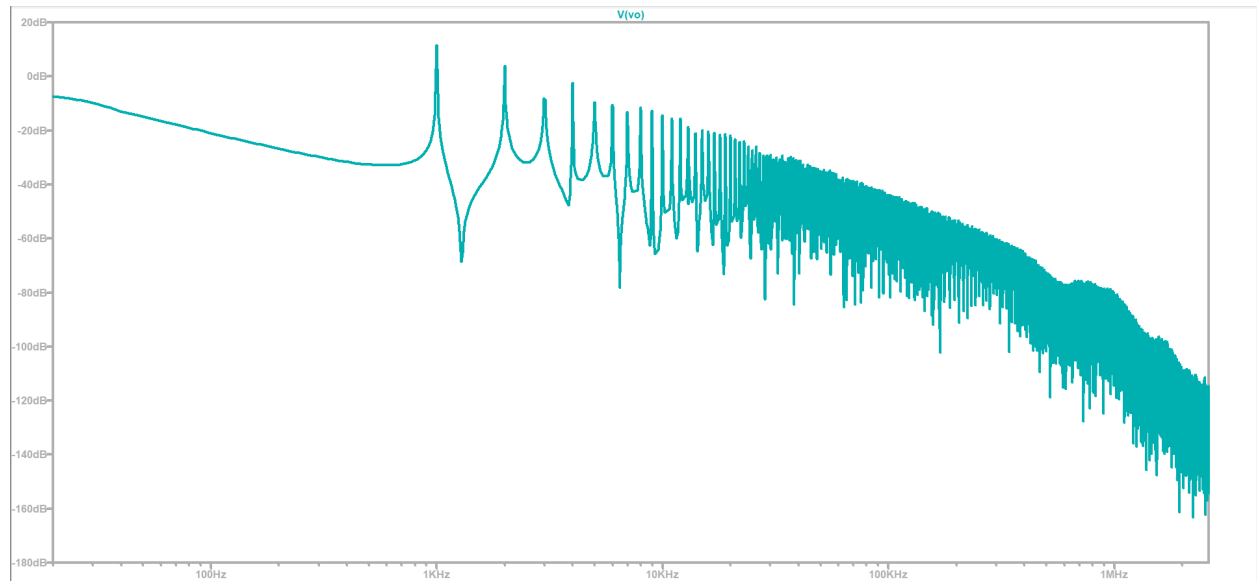

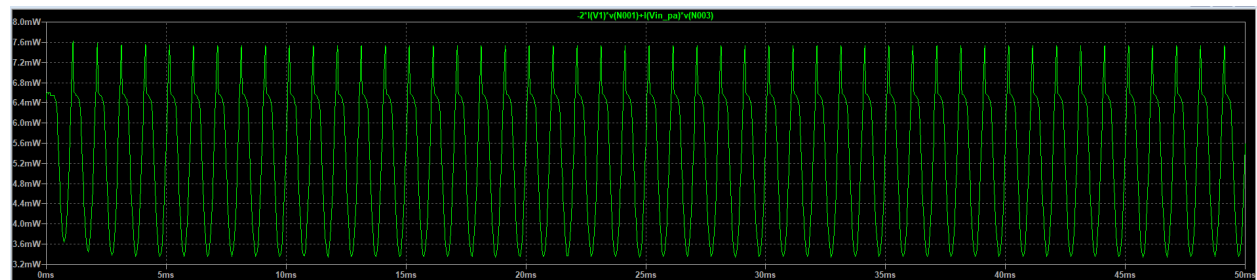Power consumption when input signal amplitude is 10 mVpp =



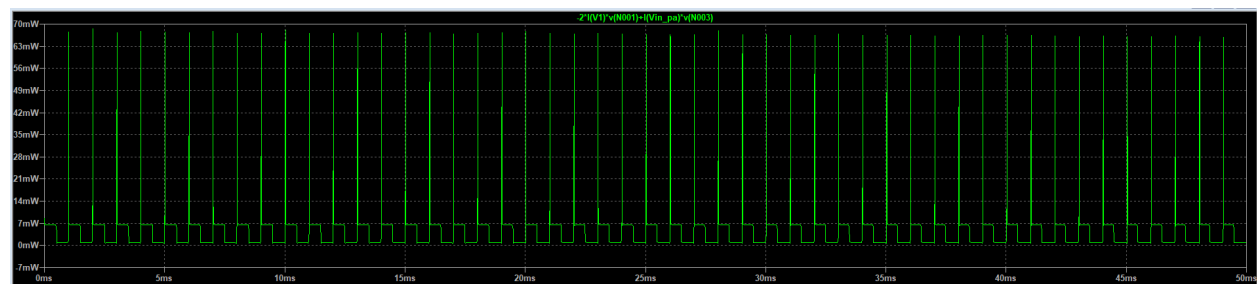
Power consumption when input signal amplitude is 1 Vpp =



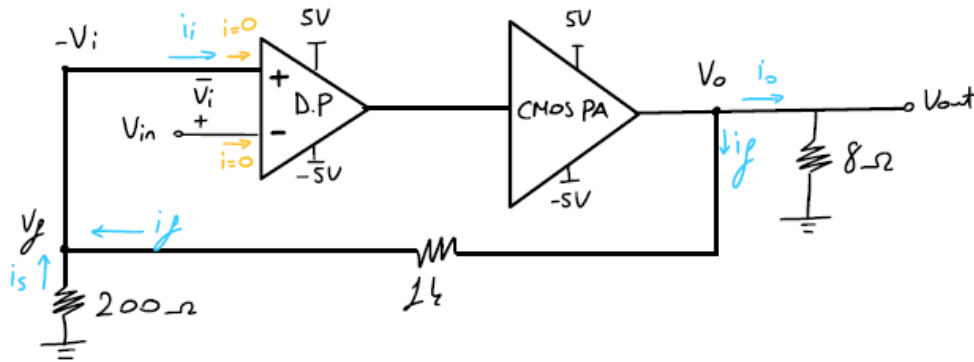3. Determine the gain of the amplifier in Figure 1. What happens to the volume that the speaker would produce when the 1-k Ω feedback resistor value is varied?

$$R_s = 200\ \Omega \quad R_f = 1\text{k}\Omega \quad R_L = 8\ \Omega$$

Series-shunt feedback (Voltage Amplifier)



$$\beta = \frac{V_f}{V_o} = \frac{R_s}{R_f + R_s} = \frac{200\ \Omega}{1\text{k}\Omega + 200\ \Omega} = \frac{1}{6} \approx 0.167$$

$$A = \frac{V_o}{V_{in}} = - \left(1 + \frac{R_f}{R_s} \right) = - \left(1 + \frac{1\text{k}\Omega}{200\ \Omega} \right) = -6$$

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A} = \frac{-6}{1 + \frac{1}{6} \cdot (-6)} \rightarrow \infty$$

If the feedback resistor value is changed the volume that the speaker will produce would be decreased as long as the feedback remains as negative feedback ($A < 0$). However, if the feedback resistor is changed to a value that the system would provide positive feedback, the volume would increase ($A > 0$).

4. The schematics in Figures 2 (a) and (b) use two supplies, 5V and -5V. This arrangement centers the output at 0V and allows us to DC couple the output stage directly to the speaker. There are cases where only a single supply is available and the speaker has to be AC coupled through a series capacitor (C_s) since the output is no longer at 0V. Determine the value for C_s for a cutoff frequency of 50 Hz or less (Hint: $f_{3dB} = 1/2\pi R_L C_s$ where R_L represents the load resistance).

$$f_{3dB} = 1/2\pi R_L C_s = 50 \text{ Hz}$$

For $R_L = 8 \Omega$ (resistance of the speaker)

$$C_s = 1/2\pi R_L f_{3dB} = 1 / ((2\pi) * 8 * 50)$$

$$\mathbf{C_s = 398 \mu F}$$